
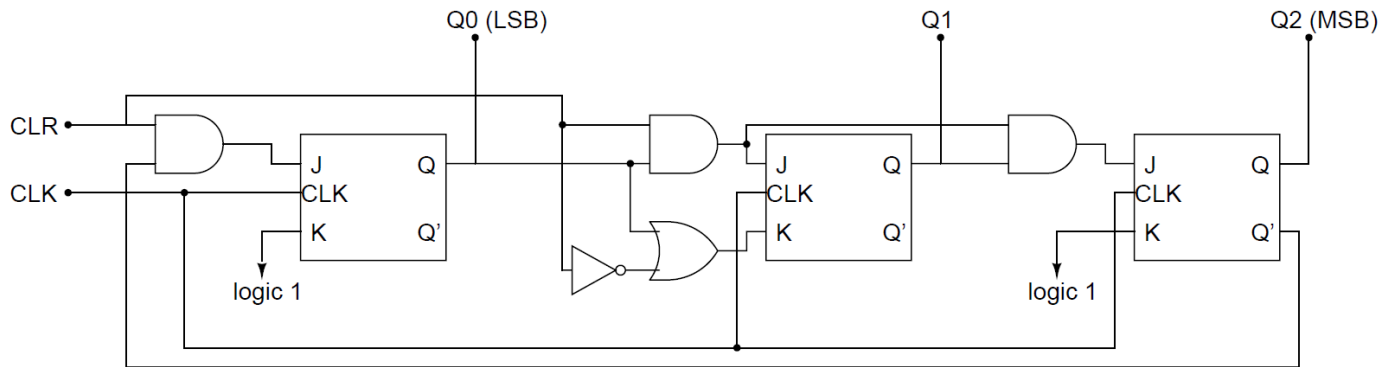


Counter Schematic


Synchronous Mod-5 Counter

 


JK FF Block



Counter schematic simulation

 

Counter post layout simulation

 


Timing analysis:

Rise time = 46.94ps

Fall time = 68.46ps

Maximum frequency of operation is around 4 GHz

 Counter simulation @ clock frequency of 4 GHz



Achieved targets:

- Final height and width of cell are 1.4um and 42.2 um respectively.
- Counter is working properly for the clock frequency of 250 MHz
- DRC (except 2) and LVS errors are cleared.

Unachieved targets:

- Two of the DRC errors (one due to low poly density and other due to low AI density) are not cleared as the design requirements of poly and AI was less than the specified value.